

CS250P: Computer Systems Architecture Pipelining



Sang-Woo Jun

Fall 2023

State of our understanding

- ❑ Complex logic has high propagation delay
 - Which leads to lower clock speed
- ❑ Naturally, we must trade-off complexity of the processor vs. clock speed
 - Is this true?

- ❑ Q1. Can we make complex processors run at higher clock speeds
- ❑ Q2. Will higher clock speeds actually lead to higher performance

Eight great ideas

- Design for Moore's Law
- Use abstraction to simplify design
- Make the common case fast
- Performance via parallelism
- Performance via pipelining
- Performance via prediction
- Hierarchy of memories
- Dependability via redundancy

But before we start...



Performance Measures

□ Two metrics when designing a system

1. Latency: The delay from when an input enters the system until its associated output is produced
2. Throughput: The rate at which inputs or outputs are processed


□ The metric to prioritize depends on the application

- Embedded system for airbag deployment? **Latency**
- General-purpose processor? **Throughput**


Performance of Combinational Circuits

□ For combinational logic

 - latency = t_{pD}
- throughput = $1/t_{pD}$



 F and G not doing work!
Just holding output data




Is this an efficient way of using hardware?


Pipelined Circuits

- Pipelining by adding registers to hold F and G's output
 - Now F & G can be working on input X_{i+1} while H is performing computation on X_i
 - A 2-stage pipeline!
 - For input X during clock cycle j, corresponding output is emitted during clock j+2.



Assuming latencies of 15, 20, 25...

 

Assuming ideal registers

 

Pipelined Circuits

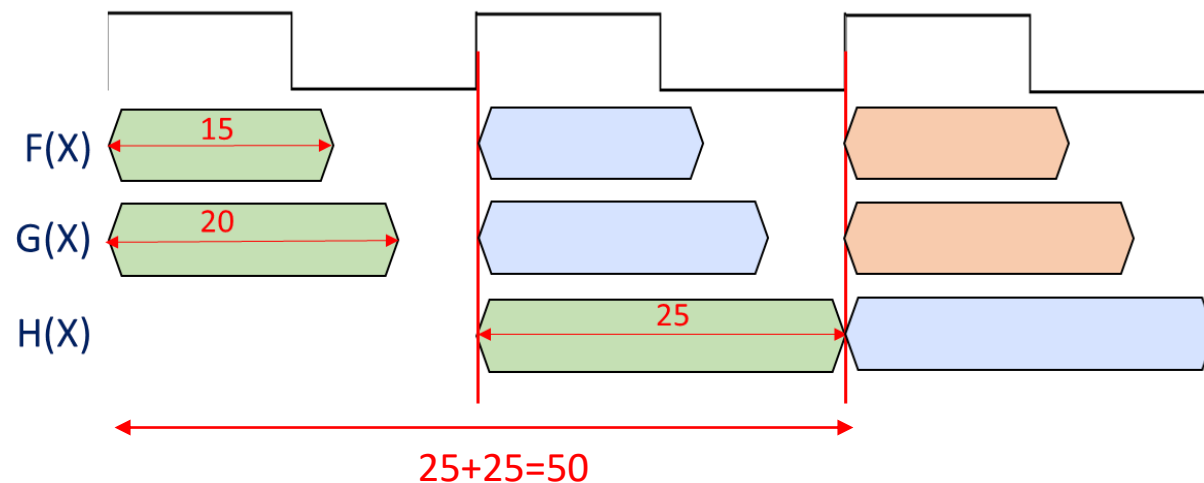 

	Latency	Throughput
Unpipelined	45	1/45
2-stage pipelined	50 (Worse!)	1/25 (Better!)

Pipeline conventions

□ Definition:

- A well-formed K-Stage Pipeline (“K-pipeline”) is an acyclic circuit having exactly K registers on every path from an input to an output.
- A combinational circuit is thus a 0-stage pipeline.

□ Composition convention:

- Every pipeline stage, hence every K-Stage pipeline, has a register on its output (not on its input).

□ Clock period:


- The clock must have a period t_{CLK} sufficient to cover the longest register to register propagation delay plus setup time.

$$\text{K-pipeline latency} = K * t_{\text{CLK}}$$

$$\text{K-pipeline throughput} = 1 / t_{\text{CLK}}$$

Ill-formed pipelines

 ❑ Is the following circuit a K-stage pipeline? No



❑ Problem:

- Some paths have different number of registers
- Values from different input sets get mixed! -> Incorrect results
 - $B(Y_{t-1}, A(X_t))$ <- Mixing values from t and t-1

A pipelining methodology

□ Step 1:


- Draw a line that crosses every output in the circuit, and mark the endpoints as terminal points.

□ Step 2:

- Continue to draw new lines between the terminal points across various circuit connections, ensuring that every connection crosses each line in the same direction.
- These lines demarcate pipeline stages.

□ Step 3:

 
- Add a pipeline register at every point where a separating line crosses a connection



Strategy: Try to break up high-latency elements, make each pipeline stage as low-latency as possible!

Pipelining example

 
- ❑ 1-pipeline improves neither L nor T
- ❑ T improved by breaking long combinational path, allowing faster clock
- ❑ Too many stages cost L, not improving T
- ❑ Back-to-back registers are sometimes needed for well-formed pipelines



	LATENCY	THROUGHPUT
0-pipe:	4	1/4
1-pipe:	4	1/4
2-pipe:	4	1/2
3-pipe:	6	1/2


Hierarchical pipelining

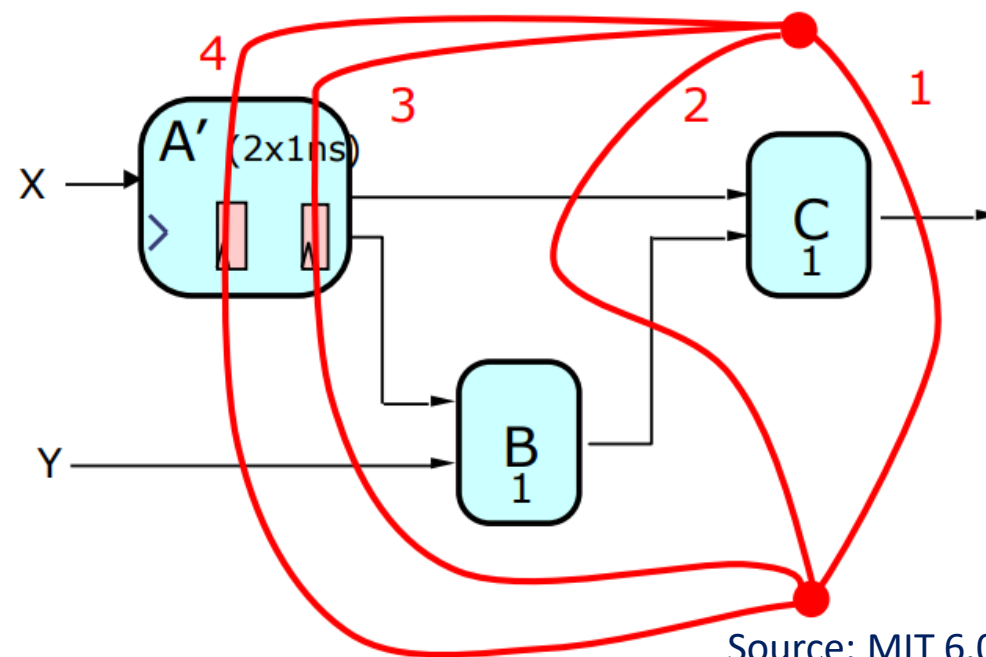- ❑ Pipelined systems can be hierarchical
 - Replacing a slow combinational component with a k-pipe version may allow faster clock
- ❑ In the example:
 - 4-stage pipeline, $T=1$



Sample pipelining problem

 - Pipeline the following circuit for maximum throughput while minimizing latency.
 - Each module is labeled with its latency




What is the best latency and throughput achievable?

Sample pipelining problem

□ $t_{\text{CLK}} = 4$


□ $T = \frac{1}{4}$

□ $L = 4 * 4 = 16$

 

Aside: When pipelines are not deterministic

- ❑ Lock-step pipelines are great when modules are deterministic
 - Good for carefully scheduled circuits like a well-optimized microprocessor
- ❑ What if the latency of F is non-deterministic?
 - At some cycles, F's pipeline register may hold invalid value
 - Pipeline register must be tagged with a valid flag
 - How many pipeline registers should we add to G? Max possible latency?
 - What if F and G are both non-deterministic? How many registers?

 


Aside: FIFOs (First-In First-Out)

❑ Queues in hardware


- Static size (because it's hardware)
- User checks whether full or empty before enqueue or dequeue
- Enqueue/dequeue in single cycle regardless of size or occupancy

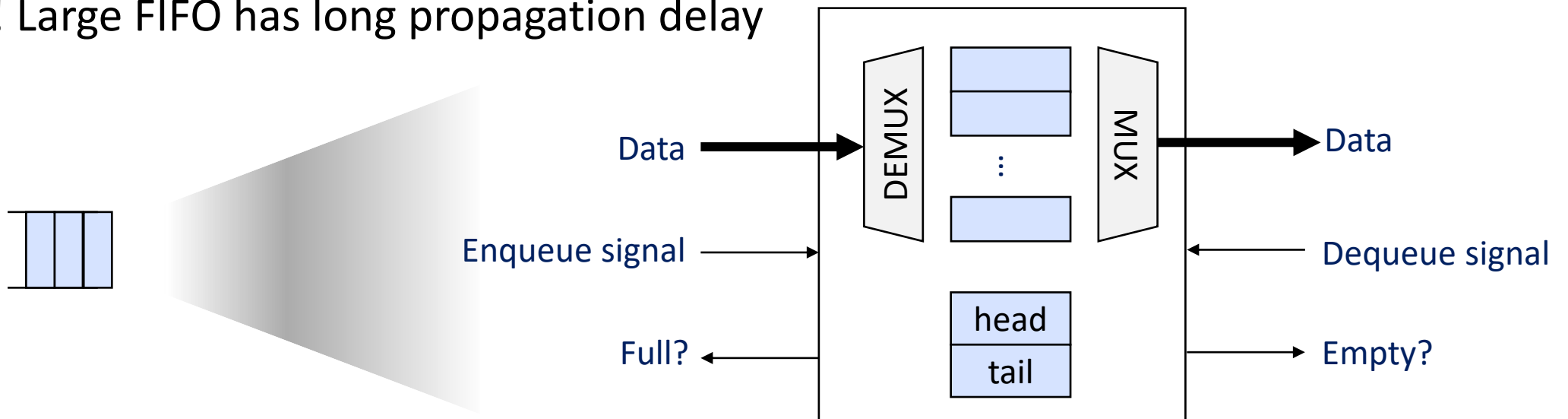- MUX! Large FIFO has long propagation delay




Counting cycles: Benefits of an elastic pipeline

- ❑ Assume F and G are multi-cycle, internally pipelined modules
 - If we don't know how many pipeline stages F or G has, how do we ensure correct results?
- ❑ Elastic pipeline allows correct results regardless of latency
 - If $L(F) == L(G)$, enqueued data available at very next cycle (acts like single register)
 - If $L(F) == L(G) + 1$, FIFO acts like two pipelined registers L <- Latency in cycles
 - What if we made a 4-element FIFO, but $L(F) == L(G) + 4$?
 - G will block! Results will still be correct!
 - ... Just slower! How slow?

 

Measuring pipeline performance

 - ❑ Latency of F is 3, Latency of G is 1, and we have a 2-element FIFO
 - What would be the performance of this pipeline?



- ❑ One pipeline “bubble” every four cycles
 - Duty cycle of $\frac{3}{4}$!

Aside: Little's law


□ $L = \lambda W$

- L: Number of requests in the system
- λ : Throughput
- W: Latency
- Imagine a DMV office! L: Number of booths. (Not number of chairs in the room)

□ In our pipeline example

- $L = 3$ (limited by pipeline depth of G)
- $W = 4$ (limited by pipeline depth of F)
- As a result: $\lambda = \frac{3}{4}$!

How do we improve performance?
Larger FIFO, or
Replicate G! (round-robin use of G1 and G2)

 

CS250P: Computer Systems Architecture

Processor Microarchitecture – Pipelining



Sang-Woo Jun

Fall 2023

Course outline

- ❑ Part 1: The Hardware-Software Interface
 - What makes a 'good' processor?
 - Assembly programming and conventions
- ❑ Part 2: Recap of digital design
 - Combinational and sequential circuits
 - How their restrictions influence processor design
- ❑ Part 3: Computer Architecture**
 - Simple and pipelined processors
 - Computer Arithmetic
 - Caches and the memory hierarchy
- ❑ Part 4: Computer Systems
 - Operating systems, Virtual memory


How to build a computing machine?

- ❑ Pretend the computers we know and love have never existed
- ❑ We want to build an automatic computing machine to solve mathematical problems
- ❑ Starting from (almost) scratch, where you have transistors and integrated circuits but no existing microarchitecture
 - No PC, no register files, no ALU
- ❑ How would you do it? Would it look similar to what we have now?

Aside: Dataflow architecture

- ❑ Instead of traversing over instructions to execute, all instructions are independent, and are each executed whenever operands are ready
 - Programs are represented as graphs (with dependency information)

 Did not achieve market success, (why?)
but the ideas are now everywhere
e.g., Out-of-Order microarchitecture



A “static” dataflow architecture


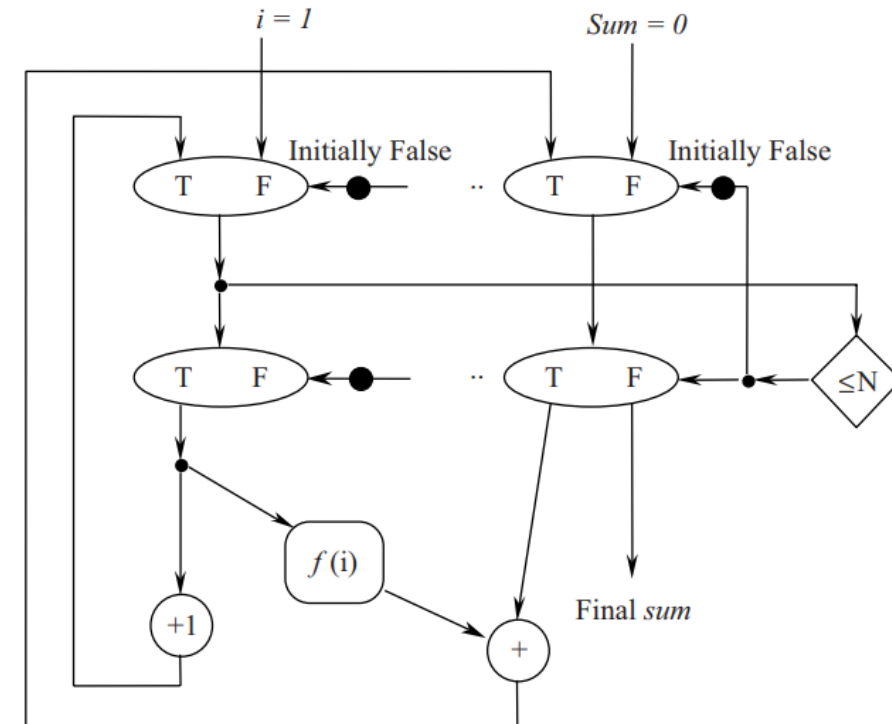


Figure 2. A dataflow graph representation of $sum = \sum_{i=1}^N f(i)$.

The von Neumann Model

- ❑ Almost all modern computers are based on the von Neumann model
 - John von Neumann, 1945
- ❑ Components
 - Main memory, where both data and programs are held
 - Processing unit, which has a program counter and ALU
 - Storage and I/O to communicate with the outside world


Key idea!

 

Key Idea: Stored-Program Computer

- ❑ Very early computers were programmed by manually adjusting switches and knobs of the individual programming elements
 - (e.g., ENIAC, 1945)
- ❑ von Neumann Machines instead had a general-purpose CPU, which loaded its instructions also from memory
 - Express a program as a sequence of coded instructions, which the CPU fetches, interprets, and executes
 - “Treating programs as data”

 
Similar in concept to a universal Turing machine (1936)



ENIAC, Source: US Army photo

 
Example: Harvard Mark 1

- ❑ Built 1944 (near the end of WW2) using switches, relays, shafts, etc
 - Used to crunch numbers for Manhattan project
 - Programmed by John von Neumann and others




 Example: Harvard Mark 1

- ❑ Slow by today standards!
 - 3 Additions/s, 6 secs for mults, etc




Data also entered via switches

 

Programs/data entered through tape,
no control flow instructions!
(Loops meant physically gluing tape into loops)

Another example: MITS Altair (1978)

 - ❑ Built using Intel 8080 @ 2 MHz
- ❑ Only input are front panel switches
- ❑ Only output are front panel LEDs
- ❑ First successful personal computer
- ❑ Bill Gates sold his first software
 - Altair BASIC
 - Tape reader expansion



EXCLUSIVE!

ALTAIR 8800

The most powerful minicomputer project ever presented—can be built for under \$400



ALTAIR 8800

BY H. EDWARD ROBERTS AND WILLIAM YATES

PROCESSOR DESCRIPTION

It's made possible by the POPULAR ELECTRONICS/MITS Altair 8800, a full- commodate 256 inputs and 256 outputs, all directly addressable, and has Processor: 8 bit parallel Max. memory: 65,000 words (all directly

Actually a bad example... Programs were entered via switches/tape but 8080 had control flow instructions!

von Neumann and Turing machine


❑ Turing machine is a mathematical model of computing machines

- Proven to be able to compute any mechanically computable functions
- Anything an algorithm can compute, it can compute

❑ Components include

- An infinite tape (like memory) and a header which can read/write a location
- A state transition diagram (like program) and a current location (like pc)
 - State transition done according to current value in tape

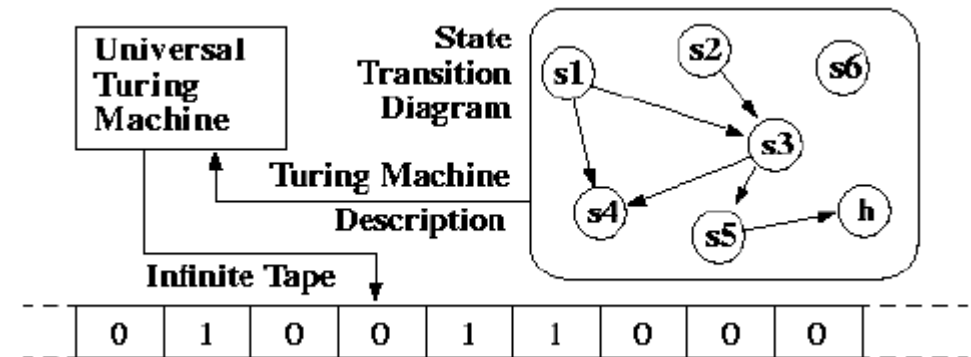❑ Only natural that computer designs gravitate towards provably universal models




Source: Manolis Kamvyselis

Stored program computer, now what?

- ❑ Once we decide on the stored program computer paradigm
 - With program counter (PC) pointing to encoded programs in memory
- ❑ Then it becomes an issue of deciding the programming abstraction
 - Instruction set architecture, which we talked about
- ❑ Then, it becomes an issue of executing it quickly and efficiently
 - Microarchitecture! – Improving performance/efficiency/etc while maintaining ISA abstraction
 - Which is the core of this class, starting now

The classic RISC pipeline

 - ❑ Many early RISC processors had very similar structure
 - MIPS, SPARC, etc...
 - Major criticism of MIPS is that it is too optimized for this 5-stage pipeline
- ❑ RISC-V is also typically taught using this structure as well



Remember:

Super simplified processor operation

```
inst = mem[PC]
```

```
next_PC = PC + 4
```

```
if ( inst.type == STORE ) mem[rf[inst.arg1]] = rf[inst.arg2]
```

```
if ( inst.type == LOAD ) rf[inst.arg1] = mem[rf[inst.arg2]]
```

```
if ( inst.type == ALU ) rf[inst.arg1] = alu(inst.op, rf[inst.arg2], rf[inst.arg3])
```

```
if ( inst.type == COND ) next_PC = rf[inst.arg1]
```

```
PC = next_PC
```

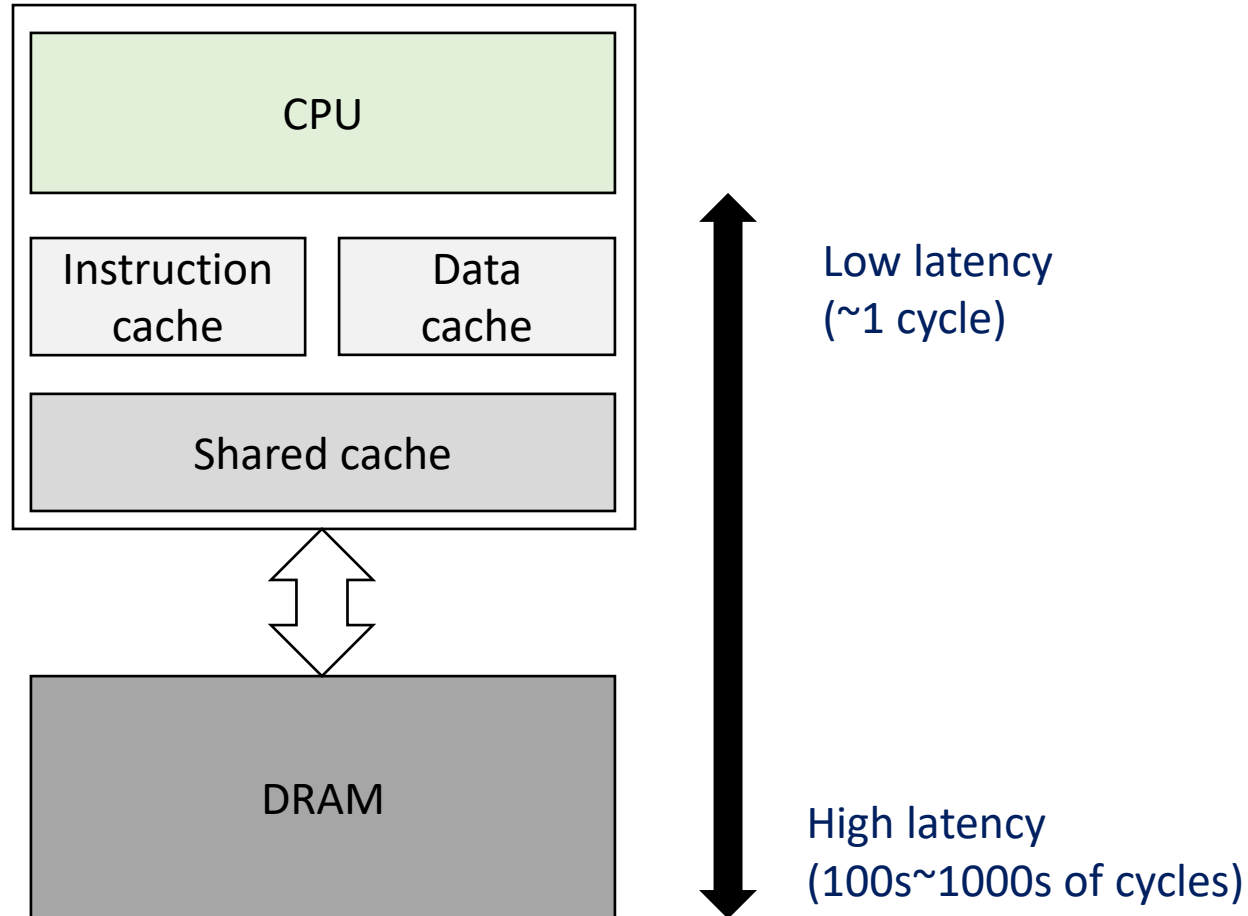

The classic RISC pipeline

- ❑ Fetch: Request instruction fetch from memory
- ❑ Decode: Instruction decode & register read
- ❑ Execute: Execute operation or calculate address
- ❑ Memory: Request memory read or write
- ❑ Writeback: Write result (either from execute or memory) back to register

Why these 5 stages? Why not 1 or 6?

Reminder:

A high-level view of computer architecture



Will deal with caches in detail later!

Designing a microprocessor

- ❑ Many, many constraints processors optimize for, but for now:


- ❑ Constraint 1: Circuit timing
 - Processors are complex! How do we organize the pipeline to process instructions as fast as possible?

- ❑ Constraint 2: Memory access latency
 - Register files can be accessed as a combinational circuit, but it is small
 - All other memory have high latency, and must be accessed in separate request/response
 - Memory can have high throughput, but also high latency

Memory will be covered in detail later!

The most basic microarchitecture

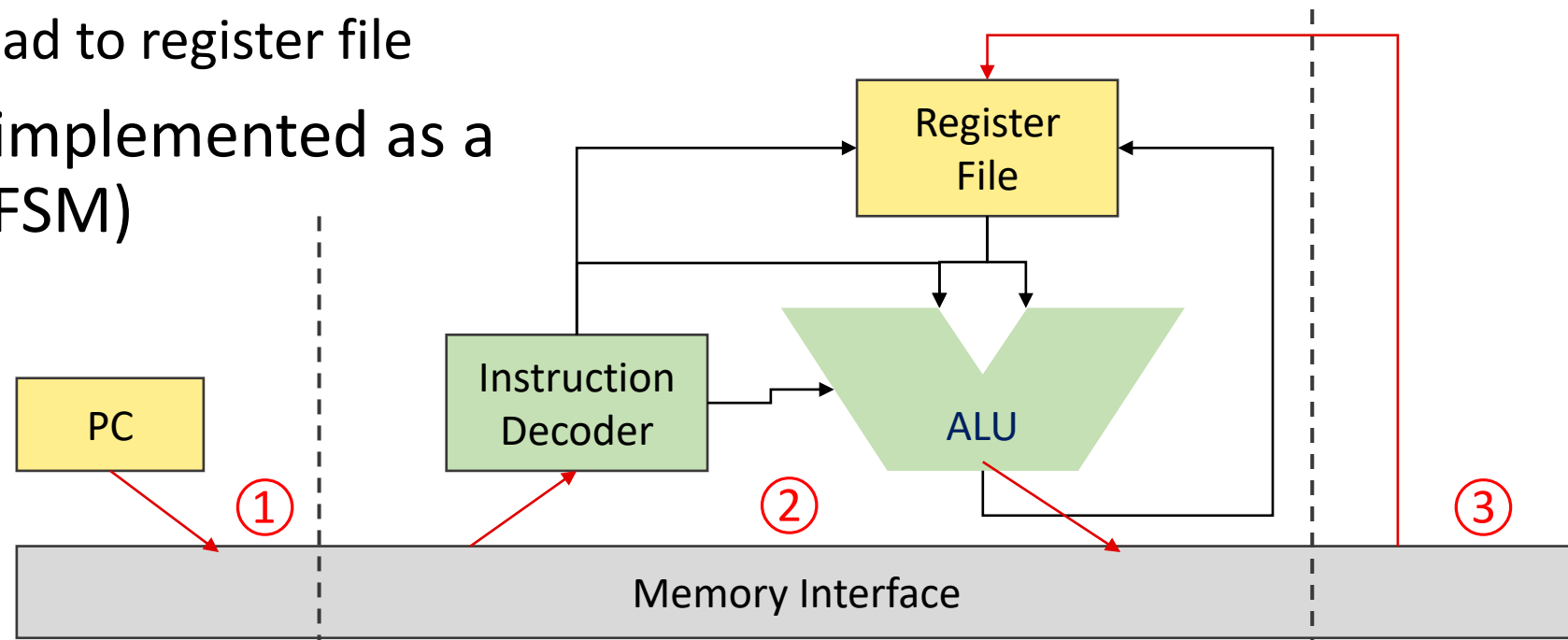
- ❑ Because memory is not combinational, our RISC ISA requires at least three disjoint stages to handle
 - Instruction fetch
 - Instruction receive, decode, execute (ALU), register file access, memory request
 - If mem read, write read to register file
- ❑ Three stages can be implemented as a Finite State Machine (FSM)



Will this processor be fast?
Why or why not?


Limitations of our simple microarchitecture

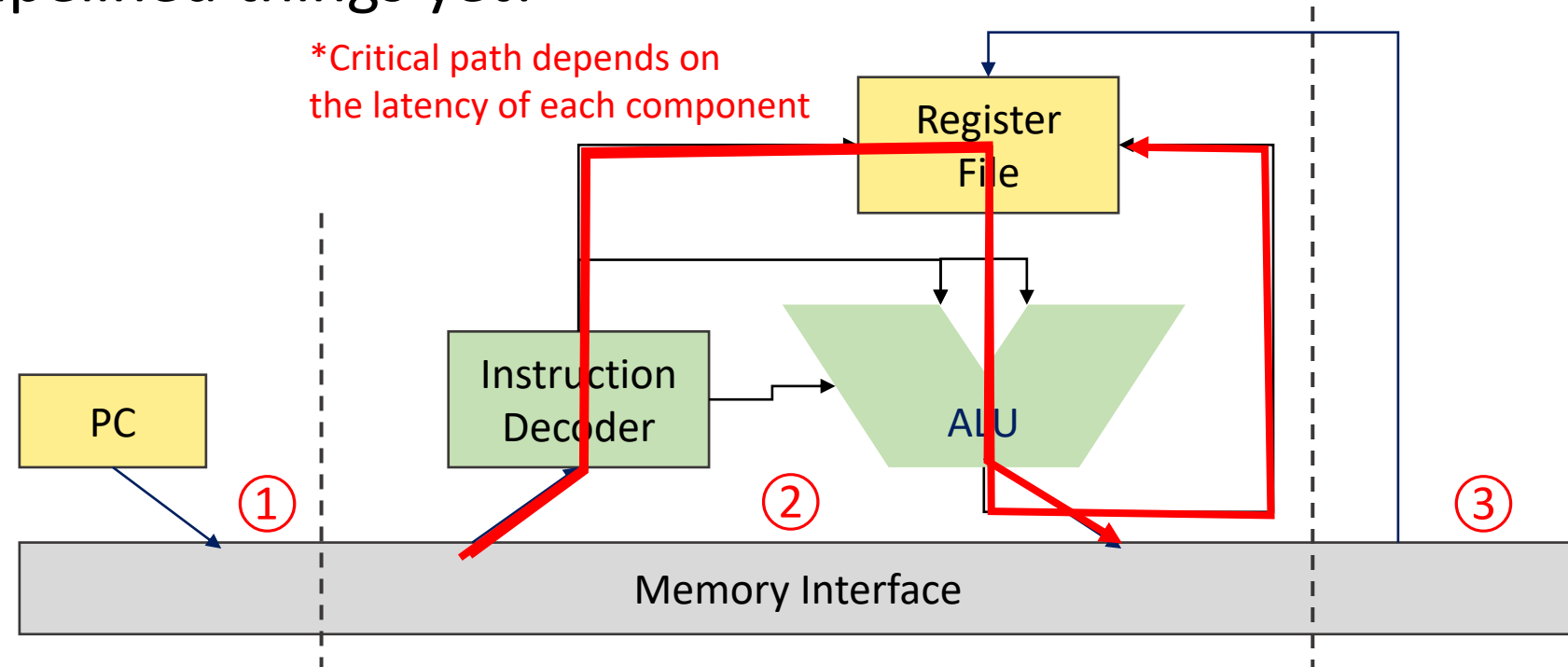- ❑ Stage two is disproportionately long
 - Very long critical path, which limits the clock speed of the whole processor
 - Stages are “not balanced”
- ❑ Note: we have not pipelined things yet!




Limitations of our simple microarchitecture

 - ❑ Let's call our stages Fetch("F"), Execute("E"), and Writeback ("W")
- ❑ Speed of our simple microarchitecture, assuming:
 - Clock-synchronous circuits, single-cycle memory
- ❑ Lots of time not spent doing useful work!
 - Can pipelining help with performance?



Pipelined processor introduction

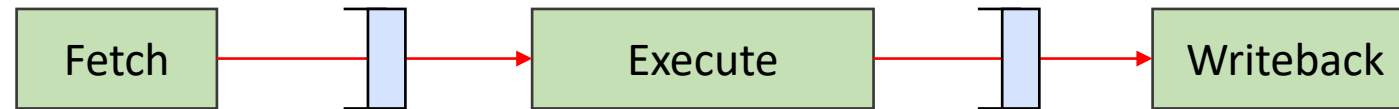
- Attempt to pipeline our processor using pipeline registers/FIFOs



* We will see soon why pipelining a processor isn't this simple

- Much better latency and throughput!

 
- Average CPI reduced from 3 to 1!
- Still lots of time spent not doing work. Can we do better?



Note we need a memory interface with two concurrent interfaces now! (For fetch and execute)
Remember instruction and data caches!


Building a balanced pipeline

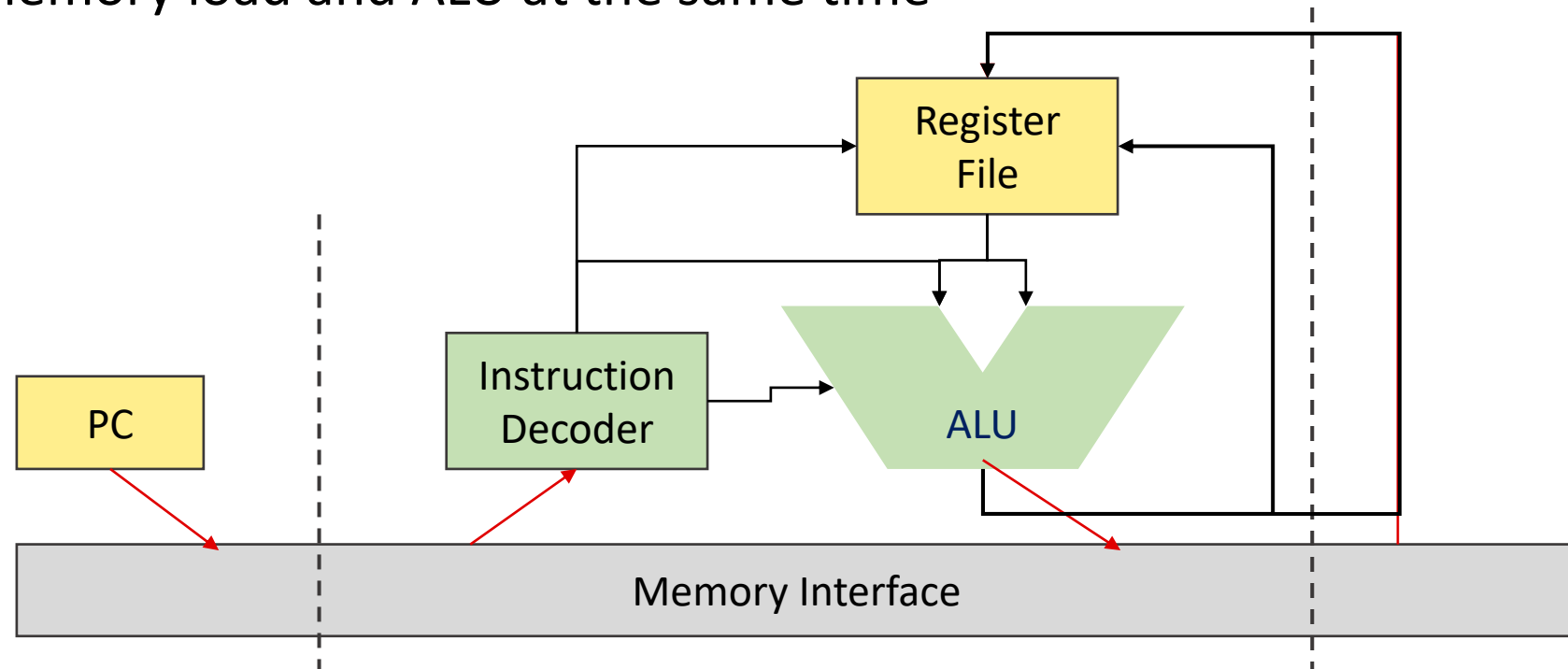- ❑ Must reduce the critical path of Execute
- ❑ Writing ALU results to register file can be moved to “Writeback”
 - Most circuitry already exists in writeback stage
 - No instruction uses memory load and ALU at the same time
 - RISC!



Building a balanced pipeline

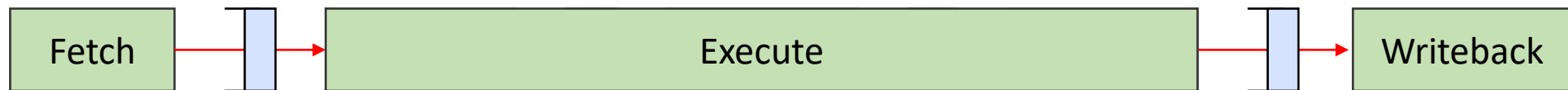
- ❑ Divide execute into multiple stages
 - “Decode”
 - Extract bit-encoded values from instruction word
 - Read register file
 - “Execute”
 - Perform ALU operations
 - “Memory”
 - Request memory read/write
- ❑ No single critical path which reads and writes to register file in one cycle



Results in a small number of stages with relatively good balance!

Ideally balanced pipeline performance

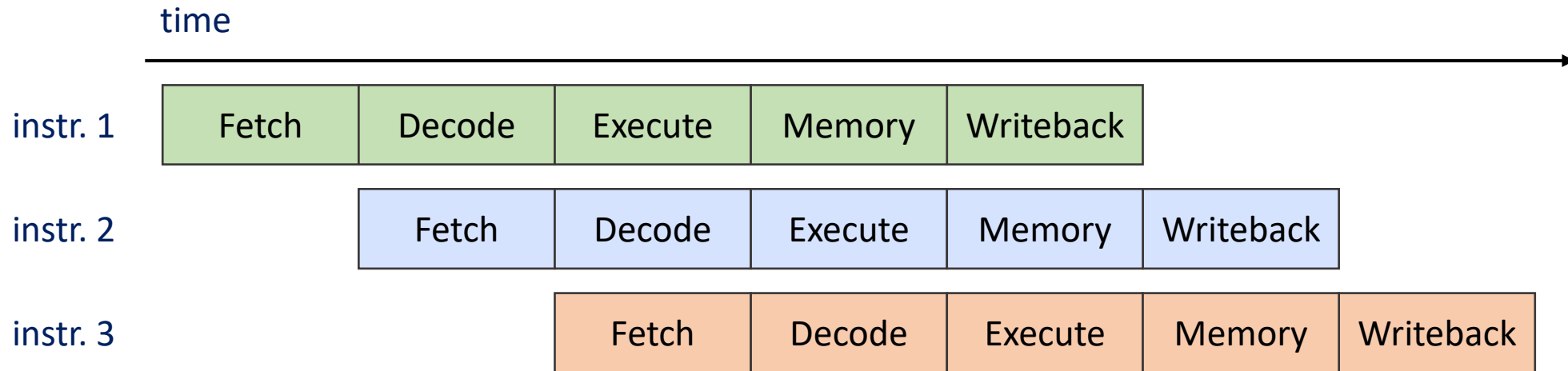- ❑ Clock cycle: 1/5 of total latency
- ❑ Circuits in all stages are always busy with useful work




Aside: Real-world processors have wide range of pipeline stages

Name	Stages
AVR/PIC microcontrollers	2
ARM Cortex-M0	3
Apple A9 (Based on ARMv8)	16
Original Intel Pentium	5
Intel Pentium 4	30+
Intel Core (i3,i5,i7,...)	14+
RISC-V Rocket	6

Designs change based on requirements!

Will our pipeline operate correctly?

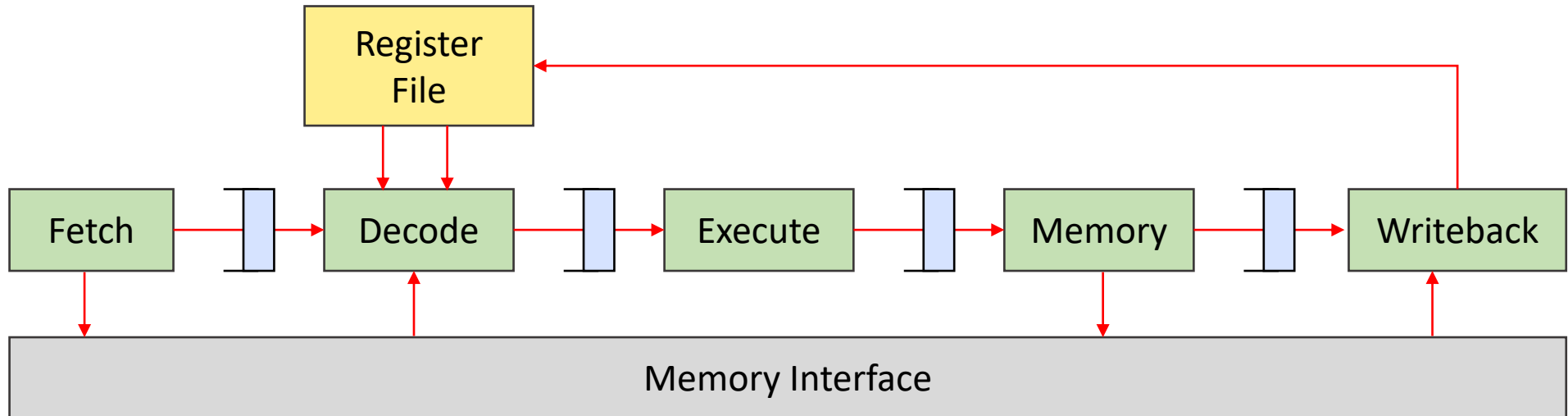

A problematic example

- ❑ What should be stored in data+8? 3, right?

```
la t0, data
lw s0, 0(t0)
lw s1, 4(t0)
add s2, s0, s1
sw s2, 8(t0)
data:
> .word 1 2
```

- ❑ Assuming zero-initialized register file, our pipeline will write zero

Why? “Hazards”